

---

# **Logic and Computer Design Fundamentals**

## **Chapter 2 – Combinational Logic Circuits**

### **Part 1 – Gate Circuits and Boolean Equations**

# Overview

---

- **Part 1 – Gate Circuits and Boolean Equations**
  - Binary Logic and Gates
  - Boolean Algebra
  - Standard Forms
- **Part 2 – Circuit Optimization**
  - Two-Level Optimization
  - Map Manipulation
  - Practical Optimization
  - Multi-Level Circuit Optimization
- **Part 3 – Additional Gates and Circuits**
  - Other Gate Types
  - Exclusive-OR Operator and Gates
  - High-Impedance Outputs

# Binary Logic and Gates

---

- Binary variables take on one of two values.
- Logical operators operate on **binary values and binary variables**.

**Basic logical operators** are the logic functions AND, OR and NOT.

- Logic gates implement logic functions.
- Boolean Algebra: a **useful mathematical system** for specifying and transforming logic functions.

We study Boolean algebra as a **foundation for** designing and analyzing **digital systems!**

# Binary Variables

---

- Recall that the **two binary values** have different names:
  - True/False
  - On/Off
  - Yes/No
  - **1/0**
- We use **1 and 0** to denote the two values.
- Variable identifier examples:
  - A, B, y, z, or  $X_1$  (**Single Letter**)
  - RESET, START\_IT, or ADD, etc

# Logical Operations

---

- The **three basic logical operations** are:
  - **AND**
  - **OR**
  - **NOT**
- **AND** is denoted by a **dot ( $\cdot$ )**.
- **OR** is denoted by a **plus ( $+$ )**.
- **NOT** is denoted by an **overbar ( $\bar{\phantom{x}}$ )**, a **single quote mark ( $'$ )** after, or ( **$\sim$** ) before the variable.

# Logical Operation Examples

---

## ■ Examples:

- $Y = A \cdot B$  is read “**Y is equal to A AND B.**”
- $z = x + y$  is read “**z is equal to x OR y.**”
- $X = \bar{A}$  is read “**X is equal to NOT A.**”

## ■ Note: The statement:

$1 + 1 = 2$  (read “**one plus one equals two**”)

is not the same as

$1 + 1 = 1$  (read “**1 or 1 equals 1**”).

# Operator Definitions

---

- Operations are defined on the values "0" and "1" for each operator:

## AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

## OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

## NOT

$$\overline{0} = 1$$

$$\overline{1} = 0$$

# Truth Tables

---

- **Truth table** – a tabular listing of the values of a **function** for **all possible combinations** of values on its **arguments**
- **Example: Truth tables for the basic logic operations:**

AND		
X	Y	$Z = X \cdot Y$
0	0	0
0	1	0
1	0	0
1	1	1

OR		
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1


NOT	
X	$Z = \overline{X}$
0	1
1	0



# Construction of Truth Table

- Determine the number of Inputs ( $n$ ) and the number of outputs ( $m$ ) according to the design requirement.
- There should be  $2^n$  rows and  $m$  output column in the Truth Table.

Input			Output
A	B	C	
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

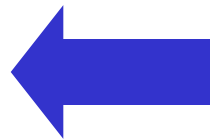

$n$			$m$		
$A_1$	...	$A_n$	$Z_1$	...	$Z_m$
0		0			
0		1			
0		0			
0		1			
1		0			
1		1			
1		0			
1		1			

$2^{n-1}$


$2^{n-1}$

# Logic Function Implementation

- In 1938, Claude E. **Shannon**, *A Symbolic Analysis of Relay and Switching Circuits*.

(He suggested that using relays to implement the logic circuits)

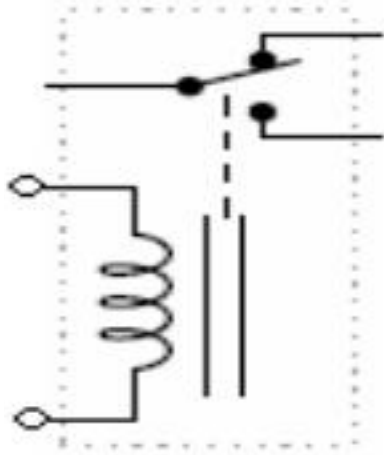- **Switches** were opened and closed by **magnetic fields** produced by energizing coils in *relays*.




# Logic Function Implementation


## ■ Using **Switches**

- For inputs:
  - logic 1 is switch closed
  - logic 0 is switch open
- For outputs:
  - logic 1 is light on
  - logic 0 is light off.
- NOT uses a switch such that:
  - logic 1 is switch open
  - logic 0 is switch closed


Switches in parallel => **OR**

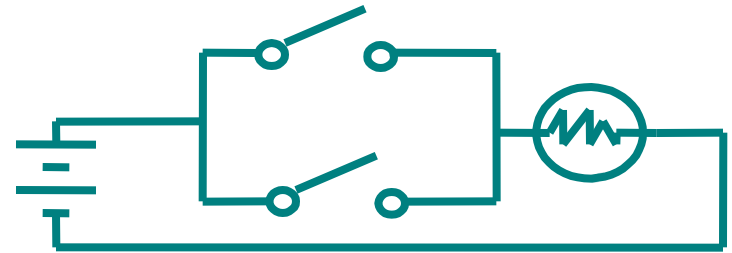

Switches in series => **AND**

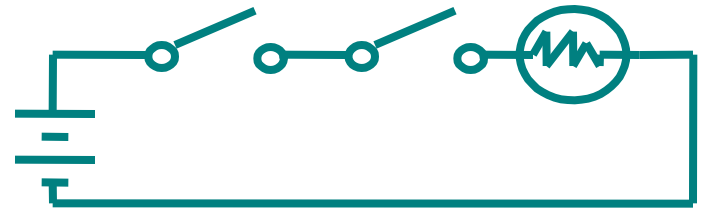


Normally-closed switch => **NOT**

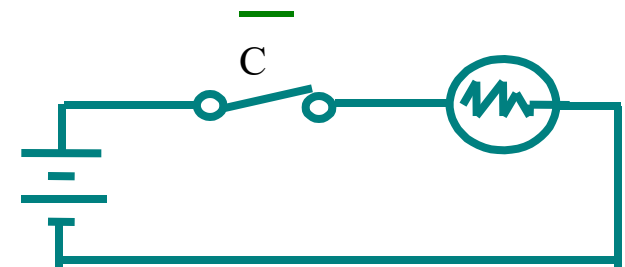

# Logic Function Implementation (Continued)

- **Example: Logic Using Switches**

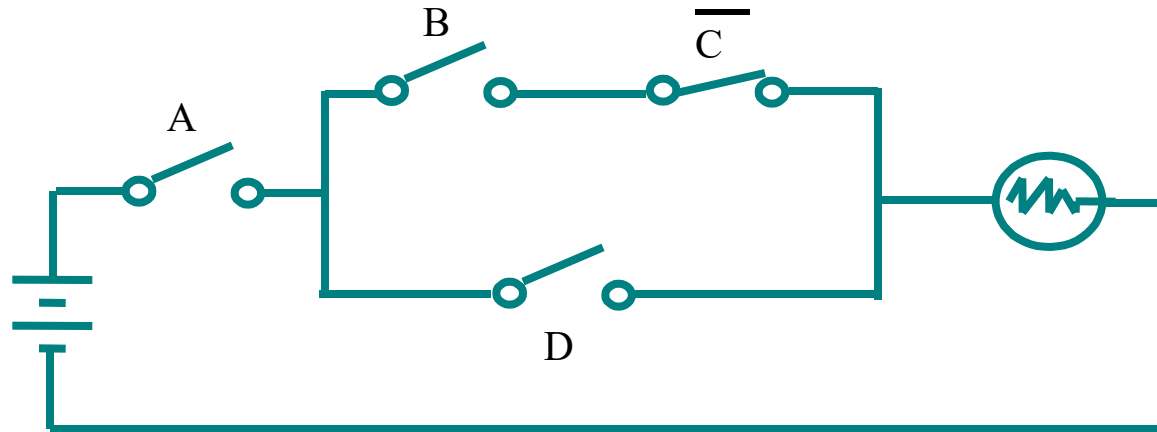


- **Light is on ( $L = 1$ ) for**

$$L(A, B, C, D) = A ((B \overline{C}) + D) = A B \overline{C} + A D$$

**and off ( $L = 0$ ), otherwise.**
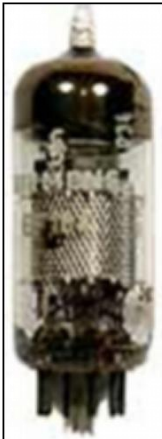
# Logic Gates

- In the earliest computers, The **magnetic-control** switches (*relays*) in turn opened and closed the current paths.
- Later, *vacuum tubes* that **open and close current paths electronically** replaced relays.
- Today, *transistors* are used as **electronic switches** that open and close current paths.



Metal Package




Plastic Package



High Power




Medium Power

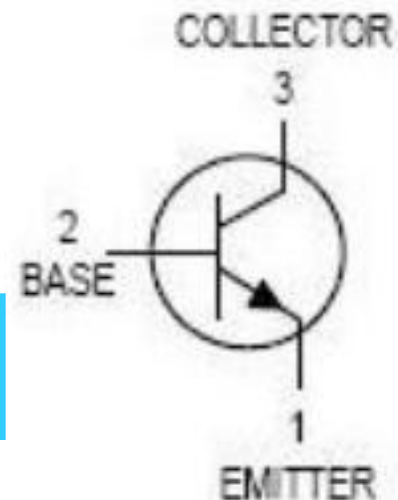


# Logic Gate Symbols and waveform Behavior

- Logic gates have **special symbols** and **waveforms** as follows:

Inputs		Output		
X	Y	$XY$	$X+Y$	$\bar{X}$
0	0	0	0	1
0	1	0	1	1
1	0	0	1	0
1	1	1	1	0

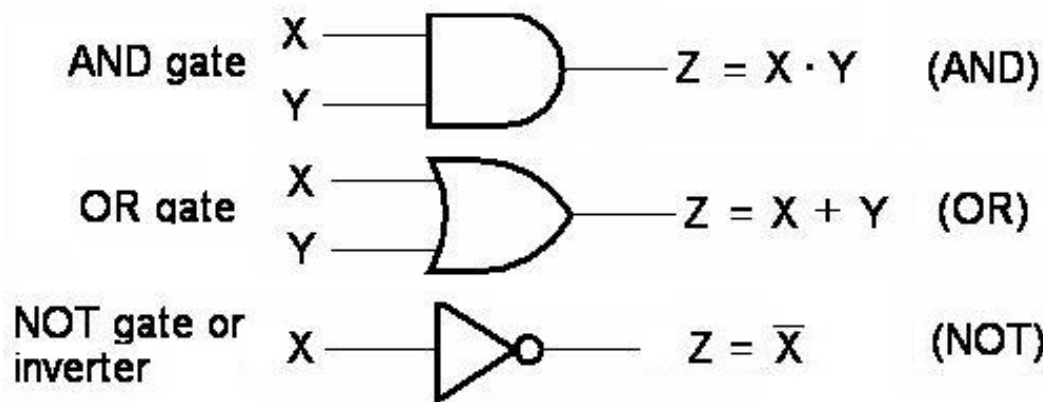

(a) Graphic symbols

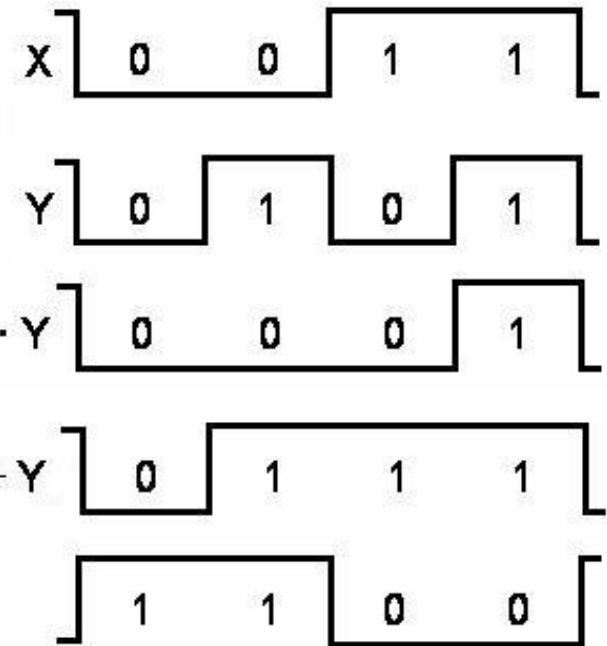

(b) Timing diagram


# Basic Gates in TTL74 Series

International



China






AND

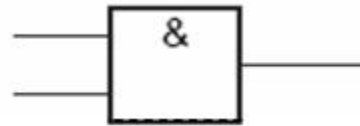

OR

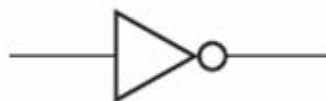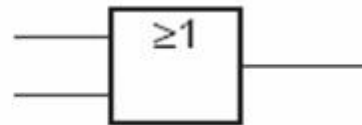


INVERTER

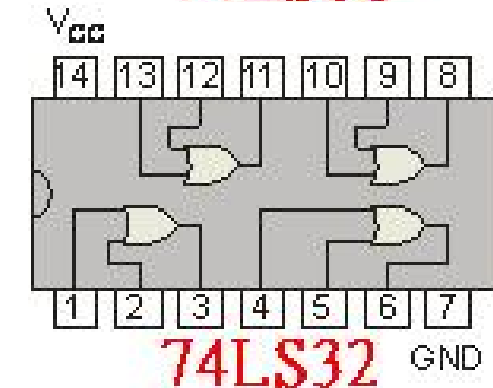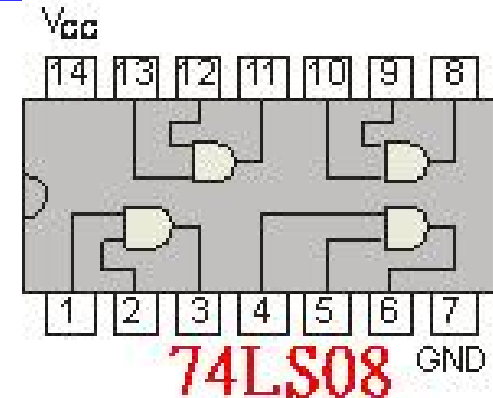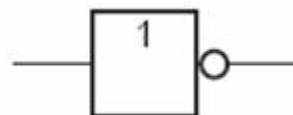
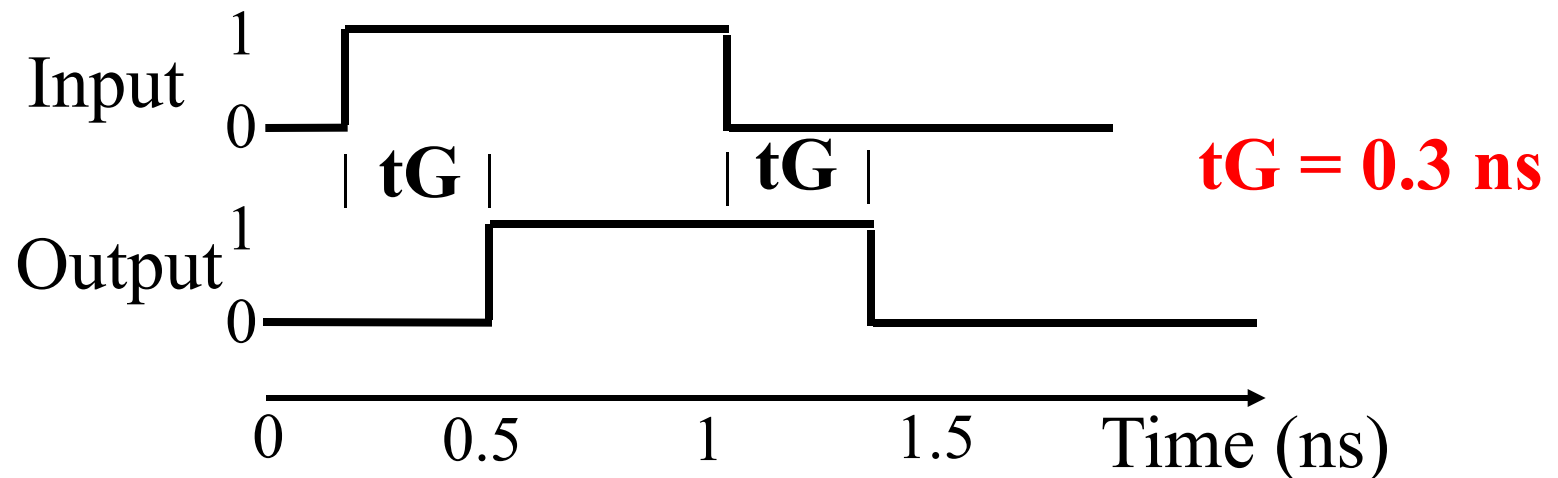
# Gate Delay


- In actual physical gates, if one or more input changes causes the output to change, the output change **does not occur instantaneously**.
- The delay between an input change(s) and the resulting output change is the *gate delay* denoted by  $t_G$ :




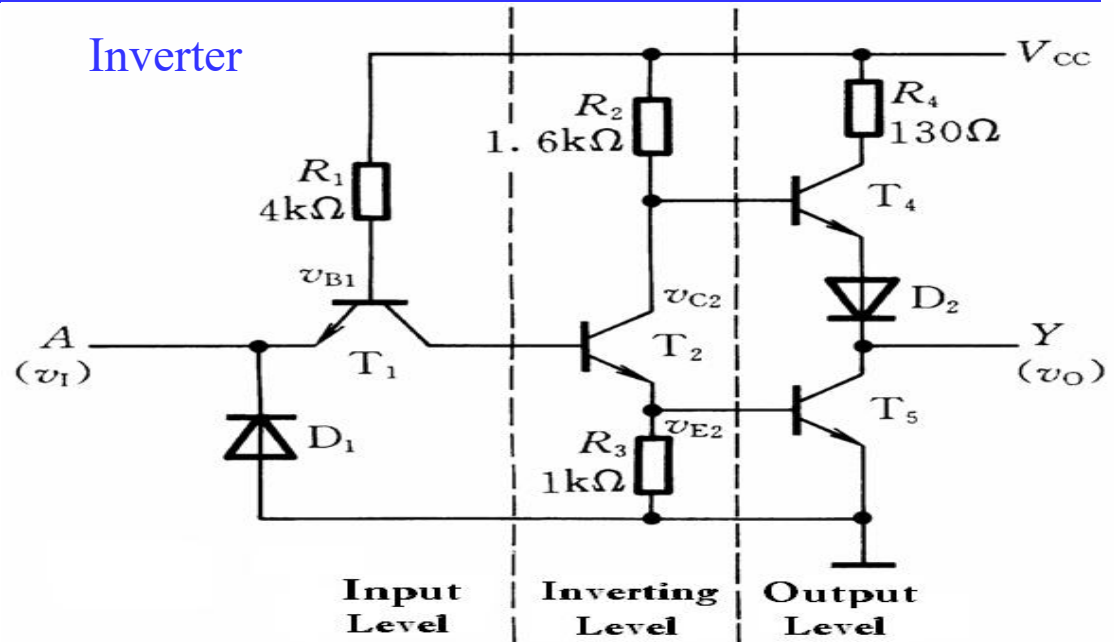
# TTL Logic Series

- 74S Series
- 74LS Series
- 74AS Series
- 74ALS Series
- 74F Series



Description	Symbol	Family				
		74S	74LS	74AS	74ALS	74F
Maximum propagation delay (ns)		3	9	1.7	4	3
Power consumption per gate (mW)		19	2	8	1.2	4
Speed-power product (pJ)		57	18	13.6	4.8	12

# Truth Table, Boolean Equation and Logic Diagram


Truth Table

X Y Z	$F = X + \bar{Y} Z$
0 0 0	0
0 0 1	1
0 1 0	0
0 1 1	0
1 0 0	1
1 0 1	1
1 1 0	1
1 1 1	1

Boolean Equation

$$F = X + \bar{Y} Z$$

Logic Diagram

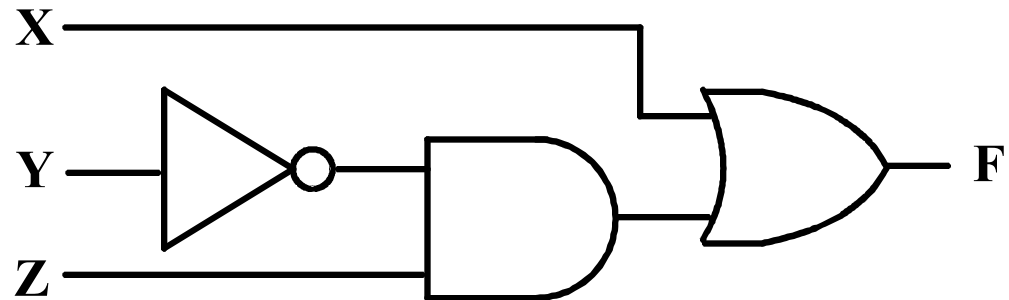

- **Boolean equations, truth tables and logic diagrams describe the same function!**
- **Truth tables are unique; Boolean equations and logic diagrams are not.** This gives flexibility in implementing functions.

# Boolean Algebra

---

In 1854, **George Boole**, *An Investigation of the Laws of Thought, on which are Founded the Mathematical Theories of Logic and Probabilities* (Idea=>0,1 symbols)

**Boolean Algebra** is **an algebraic structure** defined on a set of at least two elements, together with three binary operators (denoted  $+$ ,  $\cdot$  and  $\bar{\phantom{x}}$  )

For example,  $AB(C+D)+\bar{E}$ ,  $F = \bar{A}B+CD$  are **Boolean Expressions**.

$F=AB(C+D)+E$  is called **Boolean Equation**

# Boolean Operator Precedence

---

- **The order of evaluation in a Boolean Expression is:**
  1. Parentheses (bracket)
  2. NOT
  3. AND
  4. OR
- **NOTE: Parentheses appear around OR expressions**
- **Example:**  $F = A(B + C)(C + \overline{D})$

# Examples of Boolean Expression

---

**Example** Determine the values of  $A$ ,  $B$ , and  $C$  that make the sum term of the expression  $\bar{A} + B + \bar{C} = 0$ ?

**Solution** Each literal must = 0; therefore  $A = 1$ ,  $B = 0$  and  $C = 1$ .

**Example** What are the values of the  $A$ ,  $B$  and  $C$  if the product term of  $A.\bar{B}.\bar{C} = 1$ ?

**Solution** Each literal must = 1; therefore  $A = 1$ ,  $B = 0$  and  $C = 0$ .

# Basic Identities in Boolean Algebra

---

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A + A = A$$

$$4. A + \bar{A} = 1$$

$$9. \bar{\bar{A}} = A$$

$$5. A \cdot 1 = A$$

$$6. A \cdot 0 = 0$$

$$7. A \cdot A = A$$

$$8. A \cdot \bar{A} = 0$$

# The Dual of an algebraic expression

---

- The **Dual** of an algebraic expression is obtained by interchanging  $+$  and  $\cdot$  and interchanging 0's and 1's.
- The identities appear in **dual pairs**.

1. $A + 0 = A$	5. $A \cdot 1 = A$	$\Rightarrow$ self-dual
2. $A + 1 = 1$	6. $A \cdot 0 = 0$	
3. $A + A = A$	7. $A \cdot A = A$	$\Rightarrow$ self-dual
4. $A + \bar{A} = 1$	8. $A \cdot \bar{A} = 0$	
- If the **dual expression** = the original expression, then we call them **self-dual**.

# Examples of the Dual Expression

---

Usually, the **dual** of an expression **does not equal the expression itself**.

*Example 1* :  $F = (A + \bar{C}) \cdot B + 0$

$$\text{dual } F = (A \cdot \bar{C} + B) \cdot 1 = A \cdot \bar{C} + B$$

*Example 2* :  $G = X \cdot Y + (\overline{W + Z})$

$$\text{dual } G = ((X + Y) \cdot (\overline{W \cdot Z}))$$

*Example 3*:  $H = A \cdot B + A \cdot C + B \cdot C$

$$\text{dual } H = (A + B)(A + C)(B + C).$$



# Useful Theorem in Boolean Algebra

---

## 1. Absorption Theorem

$$A + AB = A, \quad A + \bar{A}B = A + B$$

## 2. Commutative Law

$$A+B = B+A, \quad AB = BA$$

## 3. Associative Law

$$A+(B+C) = (A+B)+C, \quad A(BC) = (AB)C$$

## 4. Distributive Law

$$A(B+C) = AB+AC, \quad A+BC=(A+B)(A+C)$$

## 5. DeMorgan Law

$$\overline{AB} = \bar{A} + \bar{B} \qquad \overline{A+B} = \bar{A}\bar{B}$$

# Application of DeMorgan Law

---

$$\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$$

$$\overline{\overline{ABC}} = A + B + C$$

$$\overline{\overline{A + B\overline{C} + D(\overline{E + \overline{F}})}}$$

$$= (A + B\overline{C})\overline{D(\overline{E + \overline{F}})}$$

$$= (A + B\overline{C})(\overline{D} + E + \overline{F})$$

# Boolean Algebraic Proof

---

- There are **two ways** to do the Proof for Boolean Identity:
  1. **Use Truth Table**, draw out the truth tables for expressions at left and right side.

If all terms of both truth tables are equal, then the expressions are identical.
  2. **Use Algebraic Manipulation**, that is to use the **identities and theorems** of Boolean algebra to make two sides equal.

# Expression to Truth Table

---

$$F1 = xy\bar{z}$$

$$F2 = x + \bar{y}z$$

$$F3 = \bar{x}\bar{y}\bar{z} + \bar{x}yz + x\bar{y}$$

$$F4 = x\bar{y} + \bar{x}z$$



x	y	z	F1	F2	F3	F4
0	0	0	0	0	1	0
0	0	1	0	1	0	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

# Proof Example of Using Truth Table

---

1. Demonstrate by means of truth table the validity of the identity:  $A + \bar{A}B = A + B$

Proof:

Write the truth tables for two sides of the Expression.

$A$	$B$	$A + \bar{A}B$	$A + B$
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	1

# Proof Example of Using Truth Table

2. Demonstrate by means of truth table the validity of the identity:  $A + B + C = \overline{A}\overline{B}\overline{C}$

**Proof:** Write the truth tables for two sides of the Expression.

$A$	$B$	$C$	$\overline{A + B + C}$	$\overline{A}\overline{B}\overline{C}$
0	0	0	1	1
0	0	1	0	0
0	1	0	0	0
0	1	1	0	0
1	0	0	0	0
1	0	1	0	0
1	1	0	0	0
1	1	1	0	0

# Proof Example of Using Algebraic Manipulation

---

1. Prove the identity of the Boolean equations,  
using algebraic manipulation:  $A + A \cdot B = A$

**Proof:**

$$L = A \cdot 1 + A \cdot B$$

$$(X = X \cdot 1)$$

$$= A \cdot (1 + B)$$

$$(X \cdot Y + X \cdot Z = X \cdot (Y + Z))$$

$$= A \cdot 1$$

$$(1 + X = 1)$$

$$= A$$

$$(X \cdot 1 = X)$$

$$= R$$

# Proof Example of Using Algebraic Manipulation

---

2. Prove the identity of the Boolean equations, using algebraic manipulation:

$$(A + B)(A + C) = A + BC$$

**Proof:**

$$\mathbf{L} = AA + AC + AB + BC$$

**(Distributive Law)**

$$= A + AC + AB + BC$$

**(X · X=1 )**

$$= A(1 + C + B) + BC$$

**(Distributive Law)**

$$= A \cdot 1 + BC$$

**(X + 1 = 1)**

$$= A + BC$$

**(X · 1=X )**

$$= \mathbf{R}$$



## Proof Example of Using Algebraic Manipulation

---

3. Prove the identity of the Boolean equations, using algebraic manipulation:

$$(\overline{A}\overline{B}(C + BD) + \overline{A}\overline{B})C = \overline{B}C$$

**Proof:**

$$\begin{aligned} & (\overline{A}\overline{B}(C + BD) + \overline{A}\overline{B})C \\ &= (\overline{A}\overline{B}C + \overline{A}\overline{B})C \\ &= (\overline{A}C + \overline{A})\overline{B}C \\ &= (\overline{A} + C)\overline{B}C \\ &= \overline{A}\overline{B}C + C\overline{B}C \\ &= \overline{B}C(\overline{A} + 1) \\ &= \overline{B}C \end{aligned}$$

# Exercise 1

---

1. Demonstrate by means of truth tables the validity of the following identities:  
(a)  $\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$       (b)  $X + YZ = (X + Y)(X + Z)$
2. Prove the identity of each of the following Boolean equations, using algebraic manipulation:  
(a)  $\overline{X}\overline{Y} + \overline{X}Y + XY = \overline{X} + Y$       (b)  $\overline{A}B + \overline{B}C + AB + \overline{B}C = 1$
3. Given that  $AB = 0$  and  $A+B=1$ , use algebraic manipulation to prove that :  $(A + C)(\overline{A} + B) = BC$

Do it manually and fill the answers in

EIE130\_Chapter2Part1\_Exercise1 via 電子作業 on  
examcoo.com

# Assignment 2

---

**2-1, 2-2, 2-4**

Due date:

D1:Next Wednesday

D2:Next Friday

During the class

# Assignment 2

---

2-1. Demonstrate by **means of truth tables** the validity of the following identities:

(a)  $\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$       (b)  $X + YZ = (X + Y)(X + Z)$

(c)  $\overline{X}Y + \overline{Y}Z + X\overline{Z} = X\overline{Y} + Y\overline{Z} + \overline{X}Z$

2-2. Prove the identity of each of the following Boolean equations, using **algebraic manipulation**:

(a)  $\overline{X} \cdot \overline{Y} + \overline{X}Y + XY = \overline{X} + Y$       (b)  $\overline{A}B + \overline{B} \cdot \overline{C} + AB + \overline{B}C = 1$

(c)  $Y + \overline{X}Z + X\overline{Y} = X + Y + Z$       (d)  $\overline{X} \cdot \overline{Y} + \overline{Y}Z + XZ + XY + Y\overline{Z} = \overline{X} \cdot \overline{Y} + XZ + Y\overline{Z}$

2-4 Given that  $AB = 0$  and  $A+B=1$ , use algebraic manipulation to prove that  $(A+C)(\overline{A}+B)(B+C) = BC$

Do it manually and fill the answers in **EIE130\_Chapter2Part1\_Assignment2** via 班級考試 on examcoo.com

# Expression Simplification

---

- **The reasons for Expression Simplification:**

1. **Reduce** the **Judgement and Program Switching** if using the software to implement the logic.
2. **Reduce** the **number of Gates and Wiring** when using the hardware to implement the logic

- **Methods of Simplification**


1. Using the **Identities and Theorem** in Boolean Algebra
2. Using the **K-map**

In this section, we only use the **first method**.

# Expression Simplification

---

- $AB + A(B+C) + B(B+C) = B + AC$

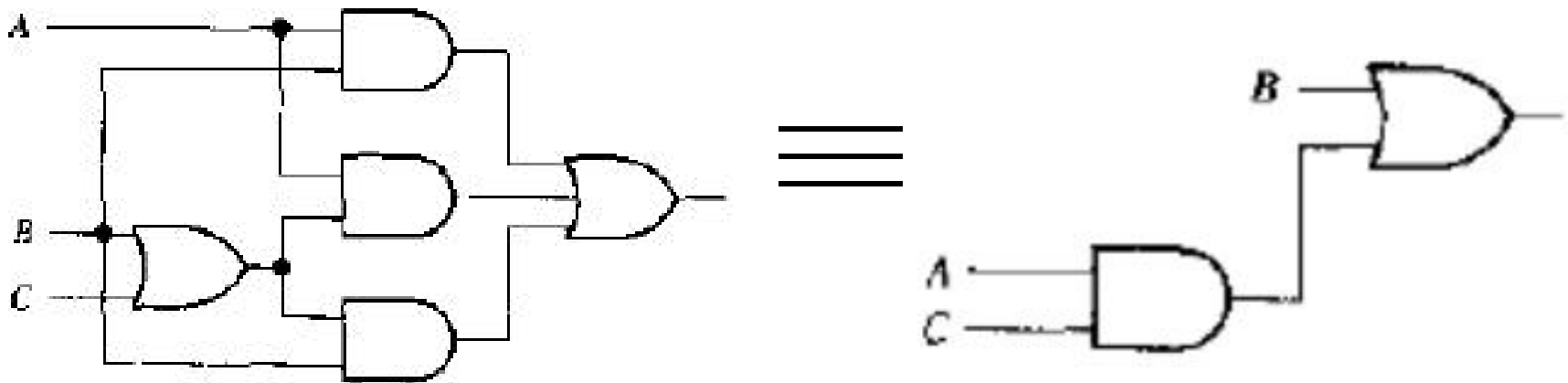

# Example of Expression Simplification

---

1. Simplify the Boolean expression to the expression containing a minimum number of literals (letter or variable)

$$\begin{aligned} & \mathbf{AB} + \bar{\mathbf{A}}\mathbf{CD} + \bar{\mathbf{A}}\mathbf{BD} + \bar{\mathbf{A}}\mathbf{C}\bar{\mathbf{D}} + \mathbf{ABCD} \\ &= \mathbf{AB} + \mathbf{ABCD} + \bar{\mathbf{A}}\mathbf{C}\mathbf{D} + \bar{\mathbf{A}}\mathbf{C}\bar{\mathbf{D}} + \bar{\mathbf{A}}\bar{\mathbf{B}}\mathbf{D} \\ &= \mathbf{AB} + \mathbf{AB}(\mathbf{CD}) + \bar{\mathbf{A}}\mathbf{C}(\mathbf{D} + \bar{\mathbf{D}}) + \bar{\mathbf{A}}\bar{\mathbf{B}}\mathbf{D} \\ &= \mathbf{AB} + \bar{\mathbf{A}}\mathbf{C} + \bar{\mathbf{A}}\bar{\mathbf{B}}\mathbf{D} = \mathbf{B}(\mathbf{A} + \bar{\mathbf{A}}\bar{\mathbf{D}}) + \bar{\mathbf{A}}\bar{\mathbf{C}} \\ &= \mathbf{B}(\mathbf{A} + \mathbf{D}) + \bar{\mathbf{A}}\bar{\mathbf{C}} \quad \mathbf{5\ literals} \end{aligned}$$

# Example of Expression Simplification

---

2. Simplify the Boolean expression to the expression containing a minimum number of literals

$$\begin{aligned} & AB + A(B + C) + B(B + C) \\ &= AB + AB + AC + BB + BC \\ &= AB + AC + B + BC \\ &= B(A + 1 + C) + AC \\ &= B + AC \end{aligned}$$

**3 literals**



# Complementing Functions

---

- Use **DeMorgan's Theorem** to complement a function:

$$\overline{AB} = \overline{A} + \overline{B}$$

$$\overline{A + B} = \overline{A}\overline{B}$$

1. Interchange AND and OR operators
2. Complement each constant value and literal

# Example of Complementing Functions

---

**Example 1: Complement**  $F = \bar{x}\bar{y}\bar{z} + x\bar{y}\bar{z}$

$$\bar{F} = (x + \bar{y} + z)(\bar{x} + y + z)$$

**Example 2: Complement**  $G = (\bar{a} + bc)\bar{d} + e$

$$\bar{G} = \overline{(\bar{a} + bc)\bar{d} + e}$$

$$= \overline{(\bar{a} + bc)\bar{d}} \cdot \bar{e}$$

$$= \overline{(\bar{a} + bc + d)} \cdot \bar{e}$$

$$= (a \cdot \bar{bc} + d) \cdot \bar{e}$$

$$= (a \cdot (\bar{b} + \bar{c}) + d) \cdot \bar{e}$$

# Exercise 2

---

1. Simplify the following Boolean expressions to expressions containing a minimum number of literals:

(a)  $\overline{A}\overline{C} + \overline{A}BC + \overline{B}C$       (b)  $\overline{(A + B + C)} \cdot \overline{ABC}$

2. Using DeMorgan's theorem, express the function

$$F = \overline{A}\overline{B}C + \overline{A}\overline{C} + AB$$

with only OR and complement operation

Do it manually and fill the answers in

EIE130\_Chapter2Part1\_Exercise2 via 電子作業 on examcoo.com

# Overview – Canonical Forms

---

- **What are Canonical Forms?**
- **Minterms and Maxterms**
- **Index Representation of Minterms and Maxterms**
- **Sum-of-Minterm (SOM) Representations**
- **Product-of-Maxterm (POM) Representations**
- **Representation of Complements of Functions**
- **Conversions between Representations**

# Canonical Forms

---

- It is useful to specify Boolean functions in a form that:
  - Allows comparison for equality.
  - Has a correspondence to the truth tables
- Canonical Forms in common usage:
  - Sum of Minterms (SOM), normally use.
  - Product of Maxterms (POM)

# Minterms

---

- Minterms are **AND terms** with every variable present in either true or complemented form.
- Given that each binary variable may appear **normal** (e.g.,  $x$ ) or **complemented** (e.g.,  $\overline{x}$ ), there are  **$2^n$  minterms for  $n$  variables**.
- Example: Two variables ( $X$  and  $Y$ ) produce  $2 \times 2 = 4$  combinations:
  - $XY$  (both normal)
  - $X \overline{Y}$  ( $X$  normal,  $Y$  complemented)
  - $\overline{X} Y$  ( $X$  complemented,  $Y$  normal)
  - $\overline{X} \overline{Y}$  (both complemented)
- Thus there are **four minterms of two variables**.

# Maxterms

---

- Maxterms are **OR terms** with every variable in true or complemented form.
- Given that each binary variable may appear normal (e.g.,  $x$ ) or complemented (e.g.,  $\bar{x}$ ), there are  **$2^n$  maxterms for  $n$  variables**.
- Example: Two variables ( $X$  and  $Y$ ) produce  $2 \times 2 = 4$  combinations:

$X + Y$  (both normal)

$X + \bar{Y}$  ( $x$  normal,  $y$  complemented)

$\bar{X} + Y$  ( $x$  complemented,  $y$  normal)

$\bar{X} + \bar{Y}$  (both complemented)

# Maxterms and Minterms

---

- **Examples: Two variable minterms and maxterms.**

Index	Minterm	Maxterm
0	$\bar{x} \bar{y}$	$x + y$
1	$\bar{x} y$	$x + \bar{y}$
2	$x \bar{y}$	$\bar{x} + y$
3	$x y$	$\bar{x} + \bar{y}$

- The **index** above is important for describing which variables in the terms are **true** and which are **complemented**.



# Standard Order

---

- All variables will be present in a minterm or maxterm and will be listed in the same order (usually alphabetically)
- *Example:* For variables a, b, c:
  - Maxterms:  $(a + b + \bar{c})$ ,  $(a + b + c)$
  - Terms:  $(b + a + c)$ ,  $a \bar{c} b$ , and  $(c + b + a)$  are NOT in standard order.
  - Minterms:  $a b c$ ,  $a \bar{b} c$ ,  $a b \bar{c}$
  - Terms:  $(\bar{a} + c)$ ,  $\bar{b} c$ , and  $(a + \bar{b})$  do not contain all variables

# Purpose of the Index

---

- The index for the minterm or maxterm, expressed as a **binary number**, is used to **determine whether the variable is shown in the true form or complemented form**.
- **For Minterms:**
  - “1” means the variable is “Not Complemented” and
  - “0” means the variable is “Complemented”.
- **For Maxterms:**
  - “0” means the variable is “Not Complemented” and
  - “1” means the variable is “Complemented”.

# Index Example in Three Variables

---

*Example for three variables:*

- Assume the variables are called  **$X$ ,  $Y$ , and  $Z$** .
- The **standard order** is  $X$ , then  $Y$ , then  $Z$ .
- The **Index 0** (base 10) = **000** (base 2) for three variables). **All** three variables **are complemented** for **minterm 0** (  $\bar{X}, \bar{Y}, \bar{Z}$ ) and **no variables are complemented** for **Maxterm 0** ( $X, Y, Z$ ).
  - Minterm **0**, called  $m_0$  is  $\bar{X}\bar{Y}\bar{Z}$ .
  - Maxterm **0**, called  $M_0$  is  $(X + Y + Z)$ .
  - Minterm **6** ?  $\Rightarrow m_6 = m_{110} \Rightarrow (XY\bar{Z})$
  - Maxterm **6** ?  $\Rightarrow M_6 = M_{110} \Rightarrow (\bar{X} + \bar{Y} + Z)$

# Index Examples in Four Variables

---

**Index    Binary    Minterm    Maxterm**

<b>i</b>	<b>Pattern</b>	<b><math>m_i</math></b>	<b><math>M_i</math></b>
<b>0</b>	<b>0000</b>	<b><math>\bar{a}\bar{b}\bar{c}\bar{d}</math></b>	<b><math>a + b + c + d</math></b>
<b>1</b>	<b>0001</b>	<b><math>\bar{a}\bar{b}\bar{c}d</math></b>	<b>?</b>
<b>3</b>	<b>0011</b>	<b>?</b>	<b><math>a + b + \bar{c} + \bar{d}</math></b>
<b>5</b>	<b>0101</b>	<b><math>\bar{a}b\bar{c}d</math></b>	<b><math>a + \bar{b} + c + \bar{d}</math></b>
<b>7</b>	<b>0111</b>	<b>?</b>	<b><math>a + \bar{b} + \bar{c} + \bar{d}</math></b>
<b>10</b>	<b>1010</b>	<b><math>a\bar{b}c\bar{d}</math></b>	<b><math>\bar{a} + b + \bar{c} + d</math></b>
<b>13</b>	<b>1101</b>	<b><math>ab\bar{c}d</math></b>	<b>?</b>
<b>15</b>	<b>1111</b>	<b><math>abcd</math></b>	<b><math>\bar{a} + \bar{b} + \bar{c} + \bar{d}</math></b>

# Minterm and Maxterm Relationship

---

- **Review: DeMorgan's Theorem**

$$\overline{xy} = \overline{x} + \overline{y} \quad \text{and} \quad \overline{x + y} = \overline{x} \cdot \overline{y}$$

- **Two-variable example (x,y) :**

$$M_2 = \overline{x} + y \quad \text{and} \quad m_2 = x \cdot y$$

$$\overline{m_2} = \overline{x \cdot y} = \overline{x} + \overline{y} = M_2$$

**Thus  $M_2$  is the complement of  $m_2$  and vice-versa.**

- Since **DeMorgan's Theorem** holds for  $n$  variables, the above holds for terms of  $n$  variables
- giving:

$$\overline{M_i} = m_i \quad \text{and} \quad \overline{m_i} = M_i$$

**Thus  $M_i$  is the complement of  $m_i$ .**

# Function Tables for Both

- **Minterms of 2 variables**

x y	m <sub>0</sub>	m <sub>1</sub>	m <sub>2</sub>	m <sub>3</sub>
0 0	1	0	0	0
0 1	0	1	0	0
1 0	0	0	1	0
1 1	0	0	0	1

- **Maxterms of 2 variables**

x y	M <sub>0</sub>	M <sub>1</sub>	M <sub>2</sub>	M <sub>3</sub>
0 0	0	1	1	1
0 1	1	0	1	1
1 0	1	1	0	1
1 1	1	1	1	0

Column

Complemented

- **Each minterm has one and only one 1 present in the  $2^n$  terms (a minimum of 1s). All other entries are 0.**
- **Each maxterm has one and only one 0 present in the  $2^n$  terms All other entries are 1 (a maximum of 1s).**

# All functions formed by two variables

---

x	y	F0	F1	F2	F3	F4	F5	F6	F7	F8	F9	F10	F11	F12	F13	F14	F15
0	0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	0	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1

**F0=0**

**F1=m0=M1xM2xM3**

**F2=m1=M0xM2xM3**

**F3=m0+m1= M2xM3**

**F4=m2=M0xM1xM3**

**.....**

**F15=1**

# Observations

---

**According to the function tables, we find that**

- We can implement any function by "ORing" the minterms corresponding to "1" entries in the function table. These are called the **minterms of the function**.
- We can implement any function by "ANDing" the maxterms corresponding to "0" entries in the function table. These are called the **maxterms of the function**.
- This gives us two canonical forms:
  - Sum of Minterms (SOM)
  - Product of Maxterms (POM)**for stating any Boolean function.**



# Minterm Function Example

Given the truth table for  $F_1$  below

We can prove that  $F_1 = m_1 + m_4 + m_7$  by substituting all the 0 and 1 in it as in the right table!

x y z	$F_1$		x y z	index	m1 + m4 + m7 = F1
0 0 0	0		0 0 0	0	0 + 0 + 0 = 0
0 0 1	1		0 0 1	1	1 + 0 + 0 = 1
0 1 0	0		0 1 0	2	0 + 0 + 0 = 0
0 1 1	0		0 1 1	3	0 + 0 + 0 = 0
1 0 0	1		1 0 0	4	0 + 1 + 0 = 1
1 0 1	0		1 0 1	5	0 + 0 + 0 = 0
1 1 0	0		1 1 0	6	0 + 0 + 0 = 0
1 1 1	1		1 1 1	7	0 + 0 + 1 = 1

$$F_1 = m_1 + m_4 + m_7$$

$$= \bar{x} \bar{y} z + x \bar{y} \bar{z} + x y z \quad ?$$

# Minterm Function Example

---

Find  $F(A, B, C, D, E) = m_2 + m_9 + m_{17} + m_{23}$

**Solution:**

$F(A, B, C, D, E) =$

$$\overline{A}\overline{B}\overline{C}\overline{D}\overline{E} + \overline{A}\overline{B}\overline{C}\overline{D}E + \overline{A}\overline{B}\overline{C}DE + \overline{A}\overline{B}CDE$$

# Maxterm Function Example

Given the truth table for  $F_1$  below

We can prove that  $F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$

by substituting all the 0 and 1 in it as in the right table!

$x \ y \ z$	$F_1$	$x \ y \ z$	$i$	$M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6 = F_1$
0 0 0	0	0 0 0	0	0 . 1 . 1 . 1 . 1 = 0
0 0 1	1	0 0 1	1	1 . 1 . 1 . 1 . 1 = 1
0 1 0	0	0 1 0	2	1 . 0 . 1 . 1 . 1 = 0
0 1 1	0	0 1 1	3	1 . 1 . 0 . 1 . 1 = 0
1 0 0	1	1 0 0	4	1 . 1 . 1 . 1 . 1 = 1
1 0 1	0	1 0 1	5	1 . 1 . 1 . 0 . 1 = 0
1 1 0	0	1 1 0	6	1 . 1 . 1 . 1 . 0 = 0
1 1 1	1	1 1 1	7	1 . 1 . 1 . 1 . 1 = 1

$$F_1 = M_0 \cdot M_2 \cdot M_3 \cdot M_5 \cdot M_6$$

$$= (x + y + z) \cdot (x + \bar{y} + z) \cdot (x + \bar{y} + \bar{z}) \cdot (\bar{x} + y + \bar{z}) \cdot (\bar{x} + \bar{y} + z)$$

# Maxterm Function Example

---

- $F(A, B, C, D) = M_3 \times M_8 \times M_{11} \times M_{14}$

**Solution:**

$$F(A, B, C, D) =$$

$$(A+B+\bar{C}+\bar{D}) \cdot (\bar{A}+B+C+D) \cdot (\bar{A}+B+\bar{C}+\bar{D}) \cdot (\bar{A}+\bar{B}+\bar{C}+D)$$

# Canonical Sum of Minterms

---

- **Any Boolean function can be expressed as a Sum of Minterms (SOM).**
- To change an expression to **Canonical Sum of Minterms**, we can expand it by “**ANDing**” any term missing a variable  $v$  with a term  $(v + \bar{v})$ .
- *Example:* Expand  $f = x + \bar{x} \bar{y}$  as a **sum of minterms**.

First expand terms:  $f = x(y + \bar{y}) + \bar{x} \bar{y}$

Then distribute terms:  $f = xy + x\bar{y} + \bar{x} \bar{y}$

Express as sum of minterms:  $f = m_3 + m_2 + m_0$

# Canonical Product of Maxterms

- **Any Boolean Function can be expressed as a Product of Maxterms (POM).**
- To change an expression to **Canonical Sum of Maxterms**, we can expand it by “**ORing**” terms missing variable  $v$  with a term  $(v \times \bar{v})$  and then applying the distributive law again.
- *Example:* Convert to product of maxterms:

$$f(x, y, z) = x + \bar{x} \bar{y}$$

Apply the distributive law:

$$x + \bar{x} \bar{y} = (x + \bar{x})(x + \bar{y}) = 1 \times (x + \bar{y}) = x + \bar{y}$$

Add missing variable  $z$ :

$$x + \bar{y} + z \times \bar{z} = (x + \bar{y} + z)(x + \bar{y} + \bar{z})$$

Express as POM:  $f = M_2 \cdot M_3$

# Shorthand SOM & POM Form

---

- To simplify the writing of the SOM and POM, we can use the Shorthand Form of them.
- Shorthand SOM Form

$$F(X_1, \dots, X_n) = \sum_m (a_1, \dots, a_n)$$

If  $F = m_1 + m_4 + m_5 + m_6 + m_7$

Then  $F(A, B, C) = \sum_m(1, 4, 5, 6, 7)$

- Shorthand POM Form

$$F(X_1, \dots, X_n) = \prod_M (a_1, \dots, a_n)$$

If  $F = M_2 M_3 M_5 M_7$

Then  $F(x, y, z) = \prod_M(2, 3, 5, 7)$

# Function Complements

---

- The **complement of a function** expressed as a sum of minterms is constructed by **selecting the minterms missing in the sum-of-minterms canonical forms**.
- Alternatively, the **complement of a function expressed by a Sum of Minterms form is simply the Product of Maxterms with the same indices**.
- *Example:* Given  $F(x, y, z) = \Sigma_m(1, 3, 5, 7)$   
 $\bar{F}(x, y, z) = \Sigma_m(0, 2, 4, 6)$   
 $\bar{F}(x, y, z) = \Pi_M(1, 3, 5, 7)$



# Conversion Between Forms

---

- To convert between **sum-of-minterms and product-of-maxterms form** (or vice-versa) we follow these steps:
  - Find the **function complement** by swapping terms in the list with terms not in the list.
  - **Change from products to sums, or vice versa.**
- *Example:* Given F as before:  $F(x, y, z) = \Sigma_m(1, 3, 5, 7)$
- Form the Complement:  $\bar{F}(x, y, z) = \Sigma_m(0, 2, 4, 6)$
- Then use the other form with the same indices – this forms the complement again, giving the other form of the original function:  $F(x, y, z) = \Pi_M(0, 2, 4, 6)$

# Standard Forms

---

- Standard Sum-of-Products (SOP) form:  
equations are written as an **OR of AND terms**
- Standard Product-of-Sums (POS) form:  
equations are written as an **AND of OR terms**
- **Examples:**
  - **SOP:**  $A B C + \bar{A} \bar{B} C + B$
  - **POS:**  $(A + B) \cdot (A + \bar{B} + \bar{C}) \cdot C$
- These **“mixed” forms** are neither SOP nor POS
  - $(A B + C) (A + C)$
  - $A B \bar{C} + A C (A + B)$

# Standard Sum-of-Products (SOP)


---

- A sum of minterms form for  $n$  variables can be written down directly from a truth table.
  - Implementation of this form is a two-level network of gates such that:
  - The first level consists of  $n$ -input AND gates, and
  - The second level is a single OR gate (with fewer than  $2^n$  inputs).
- This form often can be simplified so that the corresponding circuit is simpler.
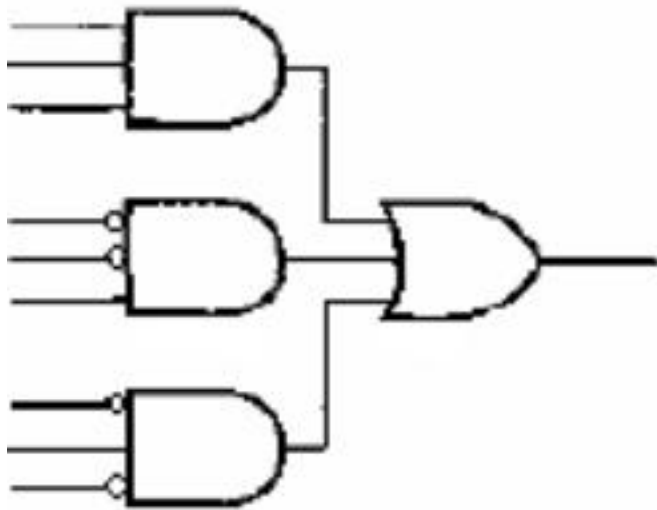
# Truth Table to Standard SOP(SOM)

- Truth Table → Standard SOP(SOM)

$$ABC + \overline{A}BC + \overline{A}B\overline{C}$$




Input			Output
A	B	C	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1
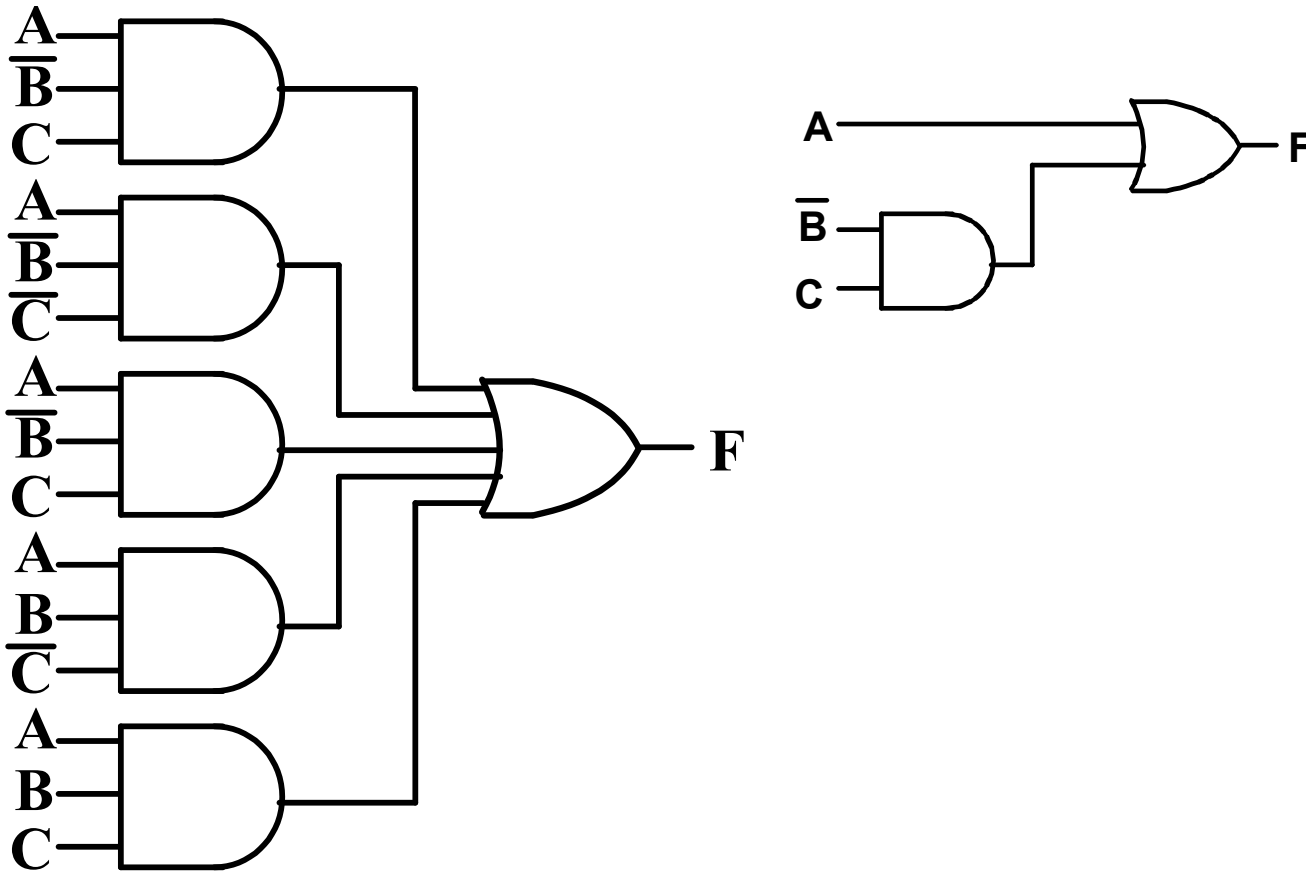
# AND/OR Two-level Implementation of SOP Expression

---

- The two level implementations for F are shown below – it is quite apparent which is simpler!



# Exercise 3

---

1. Expand  $F = A + \bar{B}C$  as a **Sum of Minterms**
2. Expand  $f(A, B, C) = A\bar{C} + BC + \bar{A}\bar{B}$  as a **Product of Maxterms**
3. **Simplify** the expression given by  
$$F(A, B, C) = \Sigma m(1, 4, 5, 6, 7)$$

Do it manually and fill the answers in

**EIE130\_Chapter2Part1\_Exercise3** via 電子作業  
on examcoo.com

# Assignment 3

---

2-6 **Simplify** the following Boolean expressions to expressions containing a minimum number of literals:

(a)  $\overline{A} \cdot \overline{C} + \overline{A}BC + \overline{B}C$     (b)  $(\overline{A+B+C}) \cdot \overline{ABC}$     (c)  $AB\overline{C} + AC$

(d)  $\overline{A} \cdot \overline{B}D + \overline{A} \cdot \overline{C}D + BD$     (e)  $(\overline{A+B})(\overline{A+C})(\overline{ABC})$

2-8 Using **DeMorgan's theorem**, express the function  $F = \overline{A}BC + \overline{A} \cdot \overline{C} + AB$

(a) with only OR and complement operations.

(b) with only AND and complement operations.

2-9 Find the complement of the following expressions:

(a)  $\overline{A}\overline{B} + \overline{A}B$     (b)  $(\overline{V}W + X)Y + \overline{Z}$

(c)  $WX(\overline{Y}Z + Y\overline{Z}) + \overline{W} \cdot \overline{X}(\overline{Y} + Z)(Y + \overline{Z})$     (d)  $(A + \overline{B} + C)(\overline{A} \cdot \overline{B} + C)(A + \overline{B} \cdot \overline{C})$

# Assignment 3

2-11 For the Boolean functions E and F, as given in the following truth table:

- (a) List the minterms and maxterms of each functions.
- (b) List the minterms of  $\overline{E}$  and  $\overline{F}$
- (c) List the minterms of  $E+F$  and  $EF$
- (d) Express  $E$  and  $F$  in sum-of-minterms algebraic form.
- (e) Simplify E and F to expressions with a minimum of literals.

Due date:

D1:Next Wednesday D2:Next Friday

Do it manually and fill the answers in

[EIE130\\_Chapter2Part1\\_Assignment3](#) via 班級考試 on examcoo.com

X	Y	Z		E	F
0	0	0		0	1
0	0	1		1	0
0	1	0		1	1
0	1	1		0	0
1	0	0		1	1
1	0	1		0	0
1	1	0		1	0
1	1	1		0	1